JF-2MED with RY-3DL

The JF-2MED can release 2 door strikes when using the RY-3DL. Wire the system as shown below to use the single door release button to activate the strike associated with the door station that is in communication with the master station.
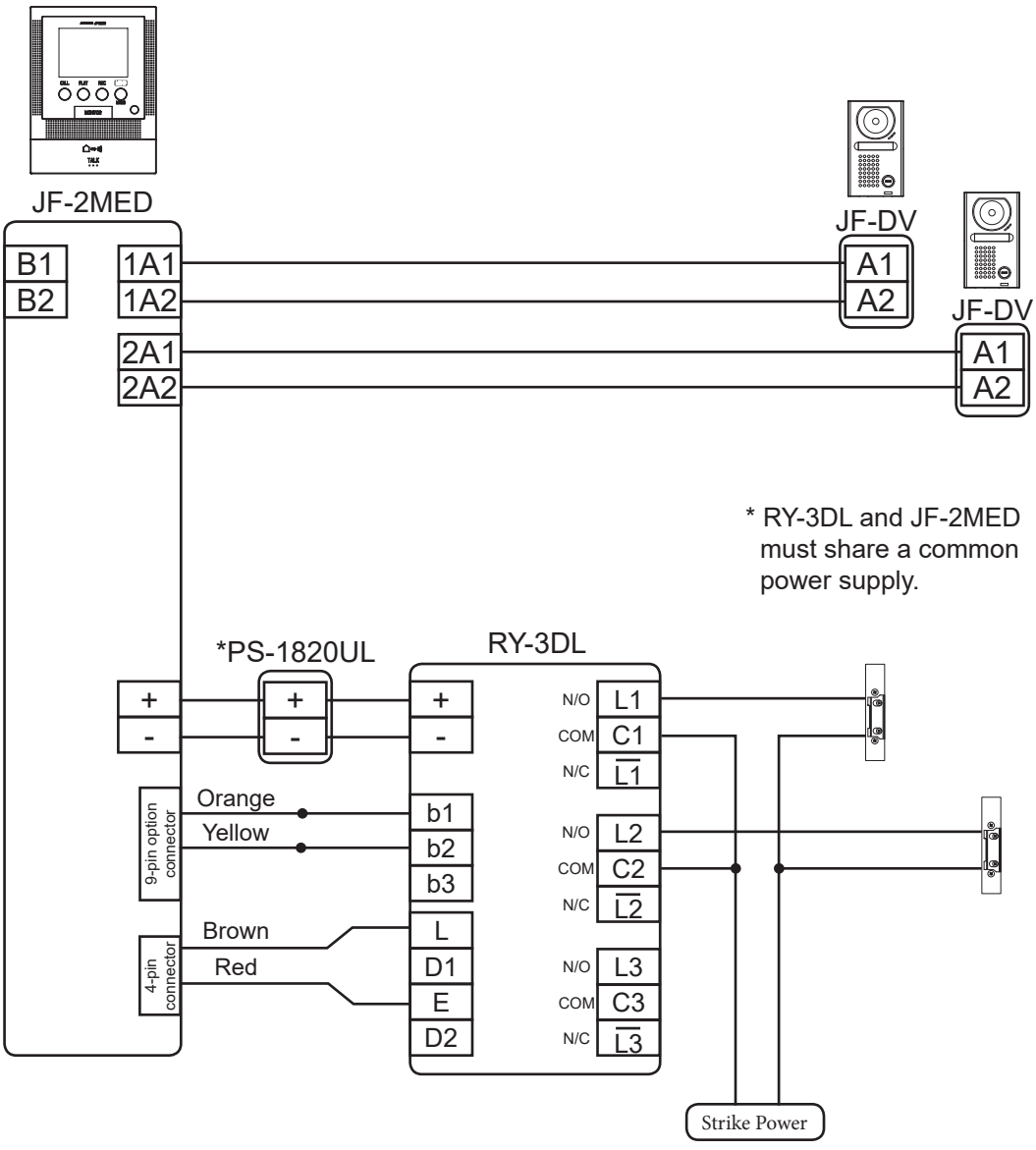
Wiring